

## Assignment 1(Spring 2020)


Circuit Theory (Phy301)

Marks: 25

Due Date: May 29, 2020

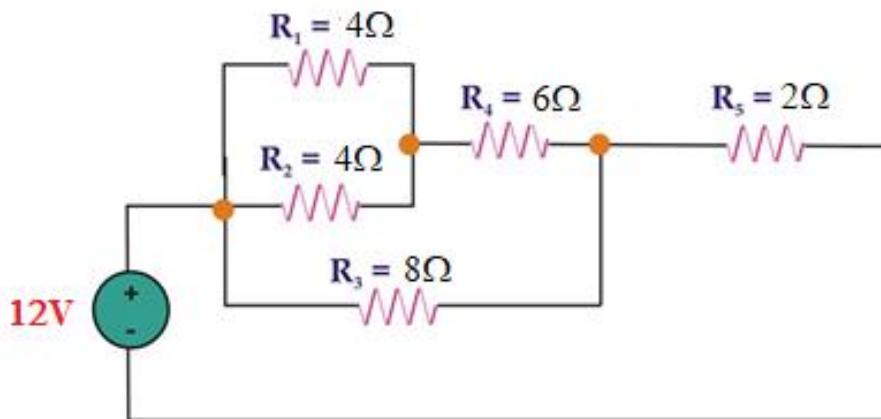**Q: 1:**

For the given below circuit, Calculate the Equivalent resistance and current of the circuit.



**Sol:**


### Calculating the Equivalent resistance

Reduce the circuit to one equivalent resistance value.

$R_1$  and  $R_2$  are connected directly in parallel and can be replaced with an equivalent resistor,

$$R_1 \text{ is parallel with } R_2 = \frac{(R_1 * R_2)}{(R_1 + R_2)}$$

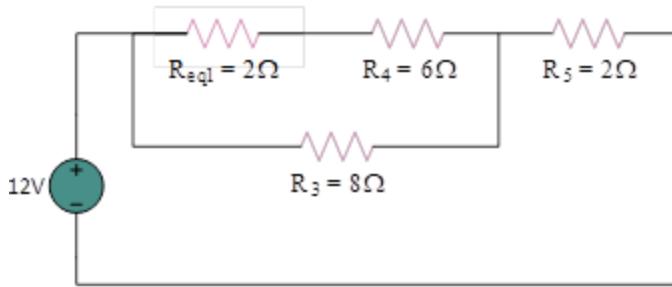
$$R_{eq1} = \frac{(4\Omega * 4\Omega)}{(4\Omega + 4\Omega)} = \frac{16\Omega}{8\Omega} = 2\Omega$$



$R_{eq1}$  is in series with  $R_4$ ,

Hence
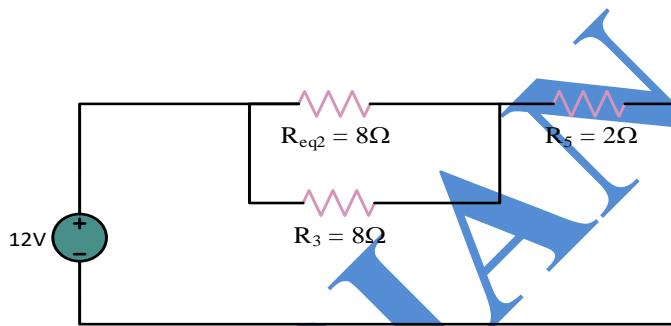
$$R_{eq2} = R_{eq1} + R_4 = 2\Omega + 6\Omega = 8\Omega$$




$R_{eq2}$  is parallel with  $R_3$ , i.e.  $R_{eq2} \parallel R_3$

So

$$R_{eq3} = \frac{(R_{eq2} * R_3)}{(R_{eq2} + R_3)}$$
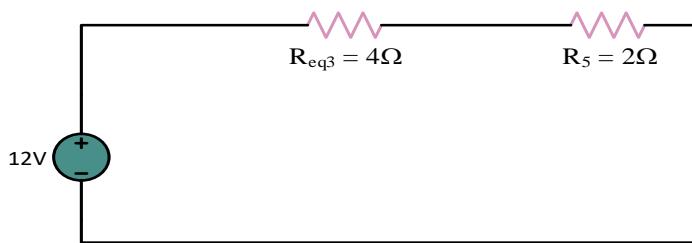
$$R_{eq3} = \frac{(8\Omega * 8\Omega)}{(8\Omega + 8\Omega)} = \frac{64\Omega}{16\Omega} = 4\Omega$$




$R_{eq3}$  is in series with  $R_5$ ,

[Cyberian.pk](http://Cyberian.pk)

So equivalent resistance is
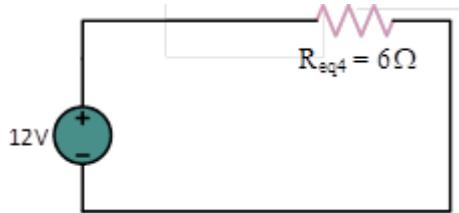
$$\begin{aligned}R_{eq4} &= R_{eq3} + R_5 = 4\Omega + 2\Omega \\&= 6\Omega\end{aligned}$$



### Finding total current

We know from ohm's law

$$V = IR$$

We have


$$V = 12V \text{ and } R = 6\Omega,$$

So total current flowing through circuit is

$$\begin{aligned}I &= \frac{V}{R} = \frac{12}{6} \\&= 2A\end{aligned}$$

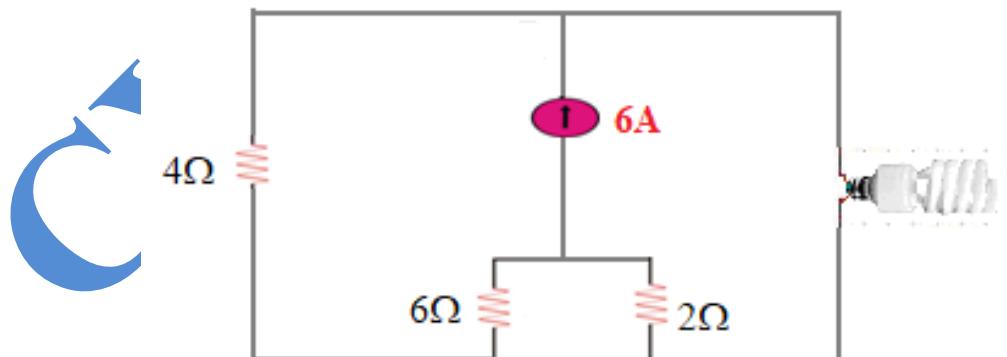
Q: 2:

Find power dissipated through energy saver having resistance  $8\Omega$ , in given below network.



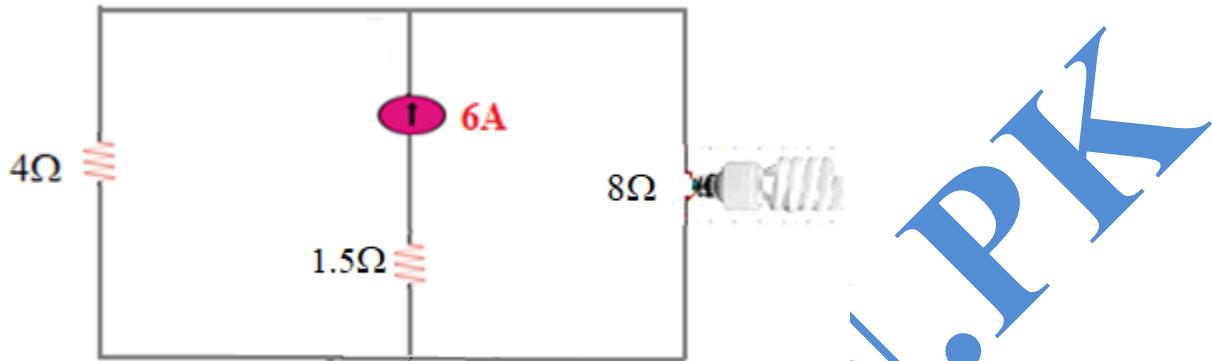**Sol;**

Since  $6\Omega$  and  $2\Omega$  are in parallel so their equivalent resistance is  $6 \times 2 / (6 + 2) = 1.5\Omega$ . Circuit can be redrawn as



We see that  $6A$  and  $1.5\Omega$  are in series so same current will pass through  $1.5\Omega$  resistance; however,  $6A$  current is divided to  $4\Omega$  and energy saver of  $8\Omega$  resistance.

Since we have to find power dissipation in  $8\Omega$  energy saver, that can be calculated by formula  $P=I^2R$  So first we find current flowing through  $8\Omega$  resistance by current divider rule as

$$I = \frac{i \times R_4}{R_t} = \frac{6 \times 4}{4 + 8}$$
$$= 2A$$

So, power dissipation through  $8\Omega$  energy saver is calculated as

$$P=I^2R$$

$$=(2)^2 8$$

$$=32W$$

**Q: 3:**

- (I) What causes positive and negative charge?
- (II) How the electrons in last orbit of an atom responsible for stability of an atom.

**Answer:**

- (I) An atom is generally considered neutral having equal no of electrons and protons. When an atom loses electron(s) it becomes positively charged and when an atom gains electron(s), it becomes negatively charged. In other words, deficiency of electron causes positive (+) charge and addition of electron causes negative (-) charge.
- (II) Electrons in outer orbit, also called valence electrons are loosely bound to its nucleus and can share to nearby outer orbit electrons of another atom. The atom is considered unstable as they share electrons to another atom. An atom of tightly bound electrons is more stable.